

# Evaluation of Subsystem Clock Oscillation Circuit

[M3823AGFFP-80P] PQFP(14x20) 0.80mm pitch

Measurement conditions :3.3V, 5.0V





Model	:SSP-T7
Frequency	:Fo=32.768kHz
Frequency tolerance	:dF/Fo= +/-20x10 <sup>6</sup>
Load capacitance	:CL=7.0pF
Equivalent series resistance	:R1=65kohm max
Max. drive level	:DL=1x10 <sup>6</sup> W max
Level of drive	:DL=0.1x10 <sup>6</sup> W typ

## FEATURES

- 1.Ultra thin type with 1.4mm Max.
- 2.SMD type suitable for automatic & high density surface mounting.
- 3.Plastic mold package containing highly reliable tubular type quartz crystal.
- 4.Excellent shock and heat resistance.
- 5.Cellular phones,PDA,Radio communication equipment, Portable applications etc.

## RECOMMENDED SOLDERING PATTERN

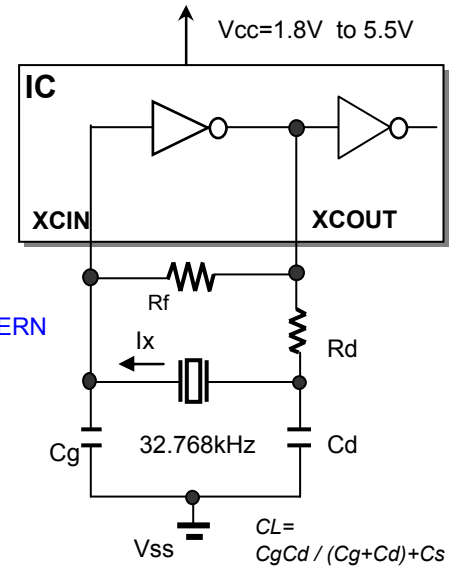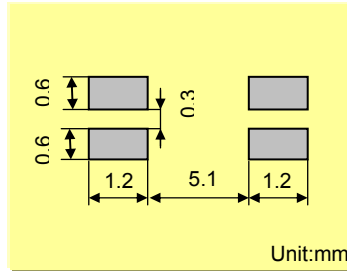

MODEL:SSP-T7 7.0pF with M3823AGFFP at 25°C

Key specifications	Vcc=3.3V	Vcc=5.0V	Remarks
Negative feedback resistance : Rf ( M ohm )	10	10	
Current control resistance : Rd ( k ohm )	220	220	Control drive level & secure phase margin
Capacitance at gate : Cg ( pF )	7	7	Optimal capacity in response to CL
Capacitance at drain : Cd ( pF )	7	7	( CL = Cd // Cg + stray capacitance )

Circuit characteristics ( at 25°C )	Vcc=3.3V	Vcc=5.0V	Remarks
Matching Accuracy : $df / f$ ( x10 <sup>-6</sup> )	-0.9	1.8	Frequency offset volume at specified Vdd
Voltage Fluctuation : $+/-df / V$ ( x10 <sup>-6</sup> )	0.5	0.6	Vdd +/-10% ( Standard operating voltage range )
Drive Level : DL ( x10 <sup>-6</sup> W )	0.05	0.05	$DL=I_x^2 R_e < 1 \times 10^{-6} W, R_e=R_1(1 + C_o / CL)^2$
Negative resistance : $ -RL $ ( kohm )	1157	1157	5 times larger than R <sub>1MAX</sub>
Oscillation allowance : M ( times )	17.8	17.8	Judgemental standard of oscillation stability
Voltage of oscillation start : Vstart ( V )	1.66	1.66	
Voltage of oscillation stop : Vstop ( V )	1.38	1.38	
Oscillation start up time : Ts ( sec )	0.52	0.49	Time to reach 90% of output level

Temperature characteristics of circuit		Vcc=3.3V	Vcc=5.0V	Remarks
at -20°C	Variation : $df / T$ ( x10 <sup>-6</sup> )	-54	-54	Typ.Tp=25°C ( K = -3.5x10 <sup>-8</sup> / °C <sup>2</sup> )
at +85°C	Variation : $df / T$ ( x10 <sup>-6</sup> )	-144	-144	Typ.Tp=25°C ( K = -3.5x10 <sup>-8</sup> / °C <sup>2</sup> )

The above mentioned value is only for your reference. The value is for the arbitrary samples and does not guarantee the product's characteristics. Please review and check above parameters at customer's end.

### Seiko Instruments USA Inc.

2990,West Lomita Blvd., Torrance, CA 90505, U.S.A  
 Telephone :+1 310-517-7771 Facsimile :+1 310-517-7792  
 Email :crystals@siu-la.com

### Seiko Instruments GmbH

Siemensstrasse 9,D-63263 Neu-Isenburg,Germany  
 Telephone :+49-6102-297-0 Facsimile :+49-6102-297-320  
 Email :info@seiko-instruments.de

### Seiko Instruments Inc.

1-8,Nakase,Mihama-ku,Chiba-shi,Chiba 261-8507,Japan  
 Facsimile :+81-43-211-8030  
 E-mail :component@sii.co.jp



We value the "takumi" spirit.







Seiko Instruments Inc.  
 Phone:+81-43-211-1207(Direct)

# Evaluation of Subsystem Clock Oscillation Circuit

[M3823AGFFP] PQFP(14x20) 0.80mm pitch  
 Measurement conditions :3.3V, 5.0V



## Test Data at 25°C

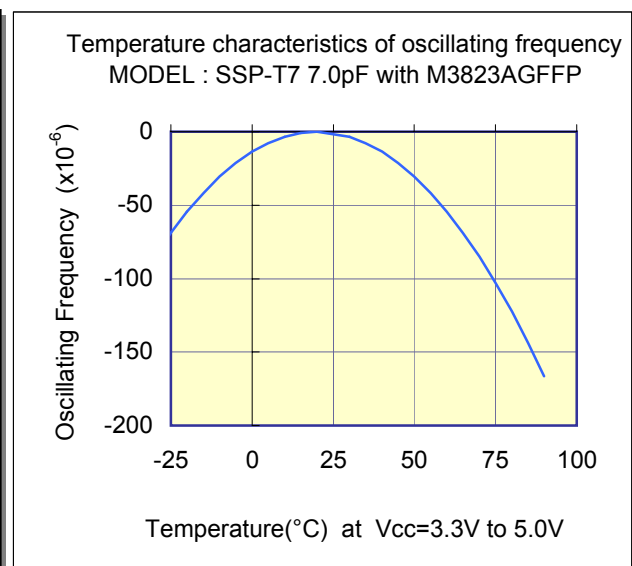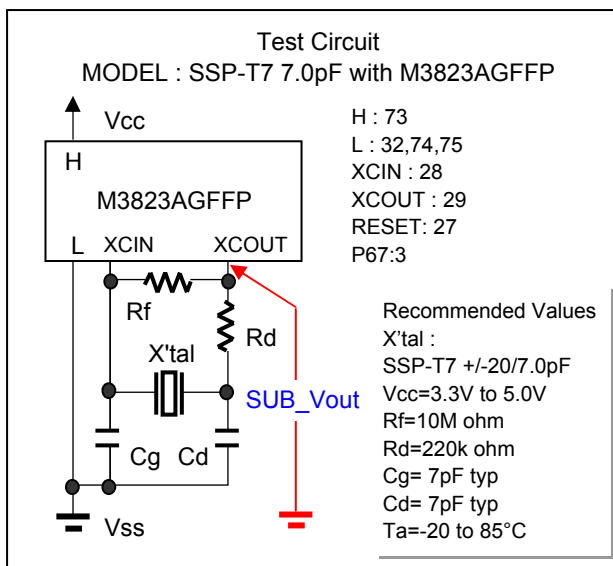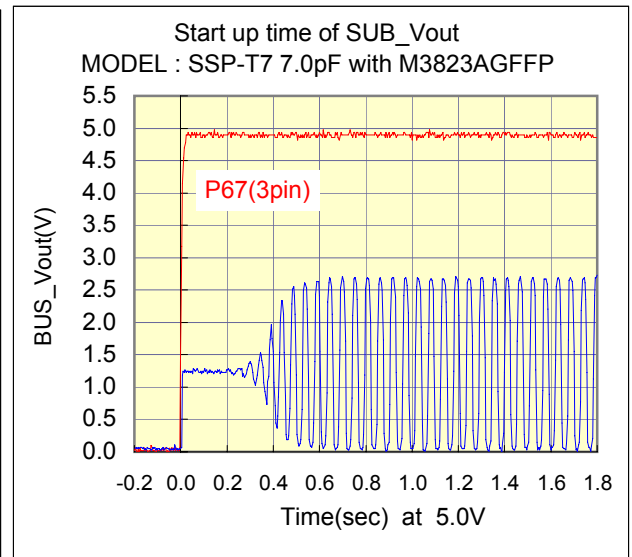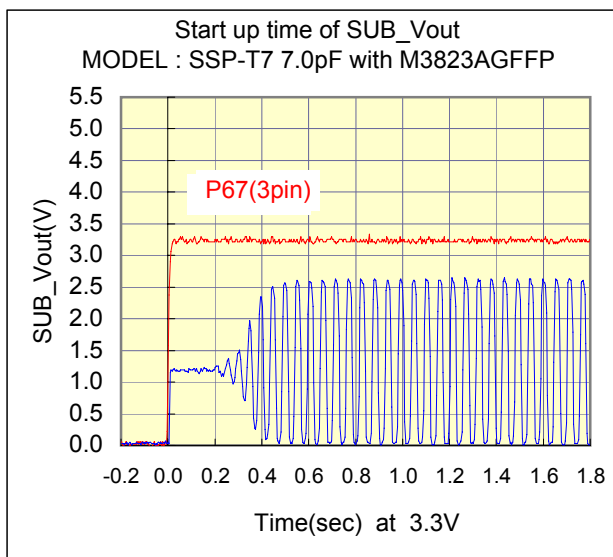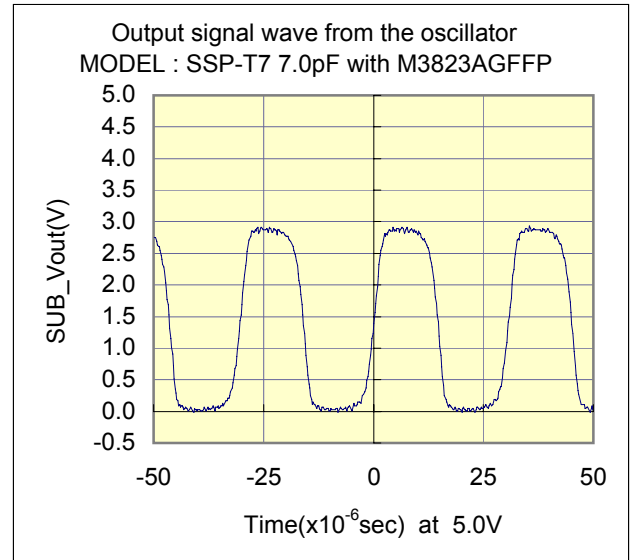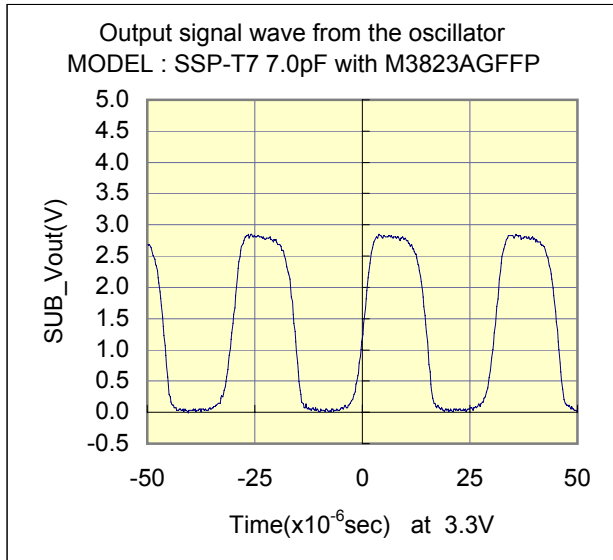







# Evaluation of Subsystem Clock Oscillation Circuit

[M3823AGFFP-80P] PQFP(14x20) 0.80mm pitch

Measurement conditions :3.3V, 5.0V


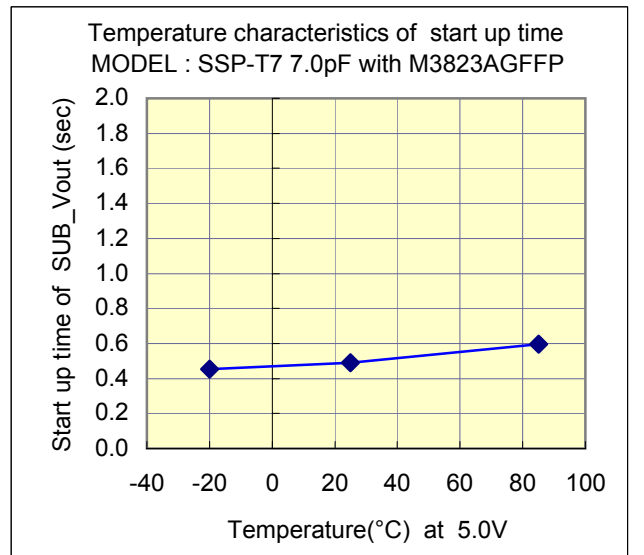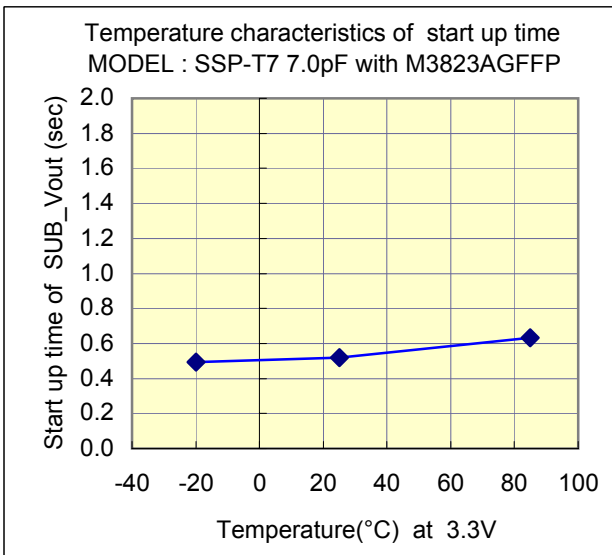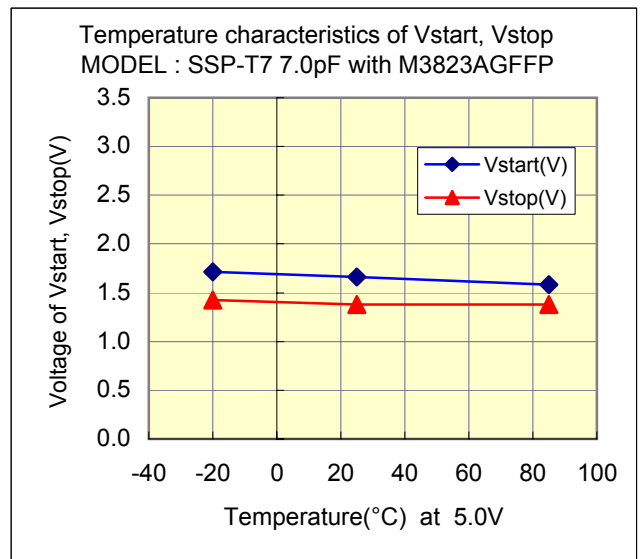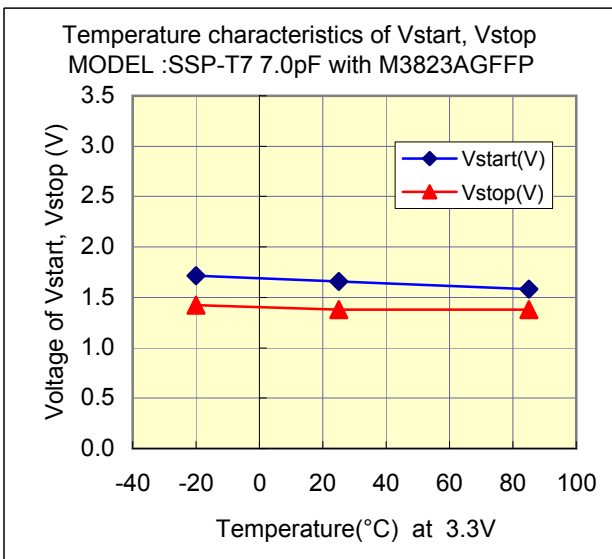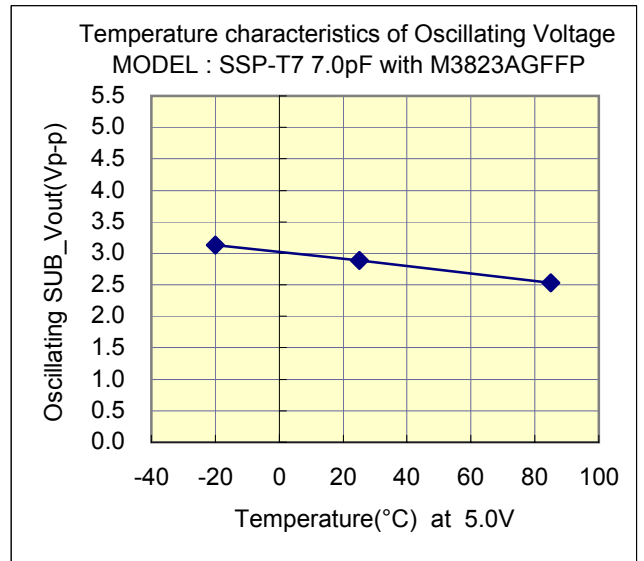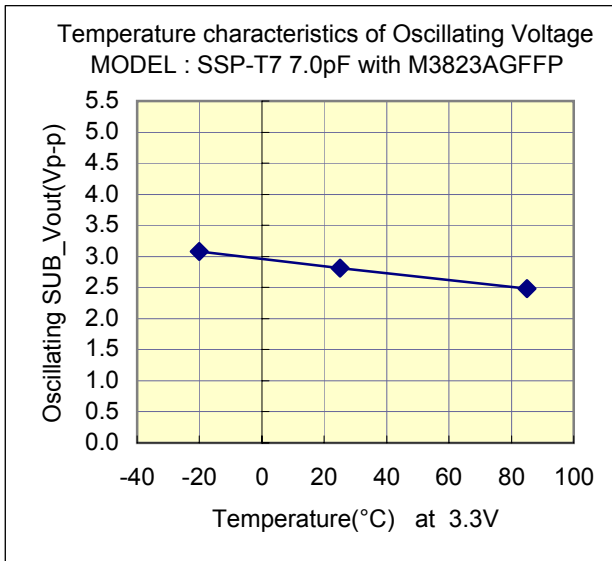
## Test Data : Temperature characteristics



# Evaluation of Subsystem Clock Oscillation Circuit

[M3823AGFFP-80P] PQFP(14x20) 0.80mm pitch

Measurement conditions :3.3V, 5.0V



## Referential components layout(see Figure 1)

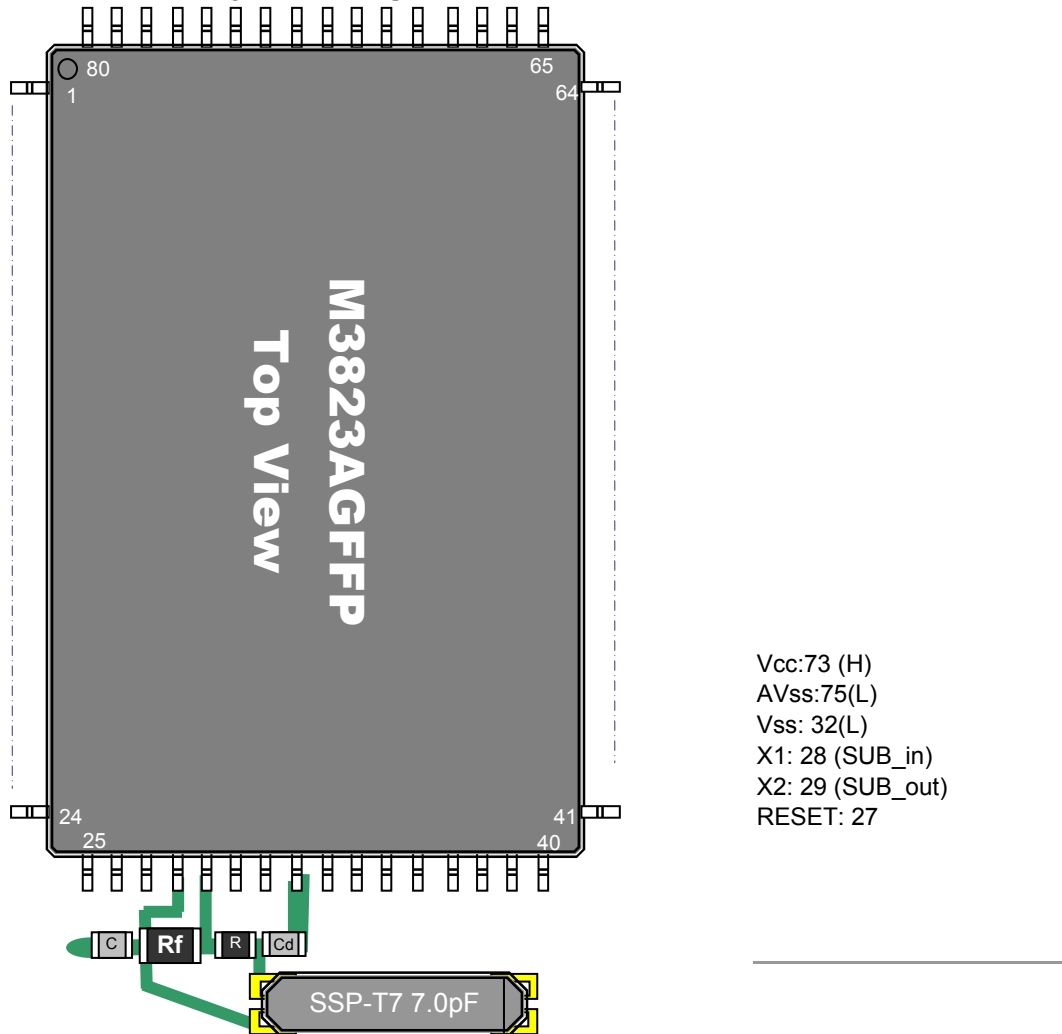


Figure 1 Referential components layout

## Notes for Board Design

When using a crystal resonator, place the resonator and its load capacitors as close as possible to SUB\_in and SUB\_out pins.

Other signal lines should be routed away from the resonator circuit to prevent induction from interfering with correct oscillation (see figure 2).

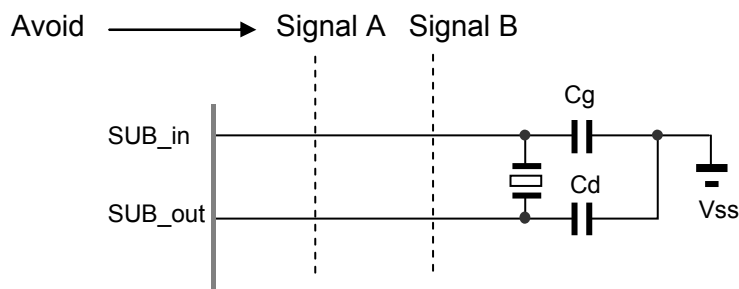


Figure 2 Example of Incorrect Board Design

**Remark** When using the subsystem clock, insert resistors  $R_d$  in series on the SUB\_out side.

# Evaluation of Subsystem Clock Oscillation Circuit

[M3823AGFFP-80P] PQFP(14x20) 0.80mm pitch

Measurement conditions :3.3V, 5.0V



## [Evaluation Sample : SSP-T7 7.0pF at 25°C]


SAMPLE	No.	CL( pF )	Fo( Hz )	fr( Hz )	R1( kohm )	Co( pF )	C1( fF )	Q( k )
SSP-T7 7.0pF	1	7	32768.40	32764.24	37.8	0.83	1.987	64.7
	2	7	32767.88	32763.63	39.2	0.85	2.037	60.9
	3	7	32767.98	32763.81	45.1	0.86	2.000	53.9

## [IC Test Data : IC samples Rf=10M ohm,Rd=220k ohm,Cg=7pF,Cd=7pF at 25°C]

Vcc(V)	IC samples	Fosc( Hz )	df / f( x10 <sup>-6</sup> )	DL(x10 <sup>-6</sup> W)	-RL  ( kohm )	Vstart( V )	Ts(sec)
5.0	TYP	32768.040	1.83	0.05	1157	1.66	0.49
	HH	32768.055	2.29	0.05	1157	1.80	0.47
	HL	32767.962	-0.55	0.05	1057	1.68	0.50
	LH	32768.110	3.97	0.04	1257	1.57	0.48
	LL	32767.956	-0.73	0.04	1257	1.44	0.44
3.3	TYP	32767.950	-0.92	0.05	1157	1.66	0.52
	HH	32767.980	0.00	0.05	1157	1.80	0.47
	HL	32767.830	-4.58	0.05	1057	1.68	0.50
	LH	32767.990	0.31	0.04	1257	1.57	0.48
	LL	32767.888	-2.81	0.04	1257	1.44	0.42
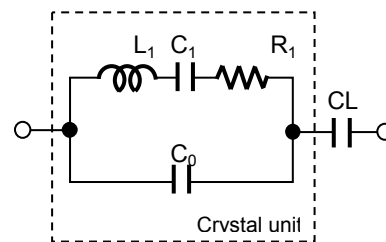
### Remark ( see figure 3 )

$$F_o = f_r \times \left\{ \frac{C_1}{2 \times (C_o + C_L)} + 1 \right\} \text{ ( Hz )}$$



Fo : Load resonance frequency  
fr : Resonance frequency  
R1 : Motional resistance  
C1 : Motional capacitance  
Co : Shunt capacitance  
CL : Load Capacitance


Figure 3 Equivalent circuit of crystal unit, and CL

### Remark ( see figure 4 )

Approximate formula of the load capacitance of the circuit CL.

$$CL = C_g \times C_d / (C_g + C_d) + C_s \text{ ( pF )}$$

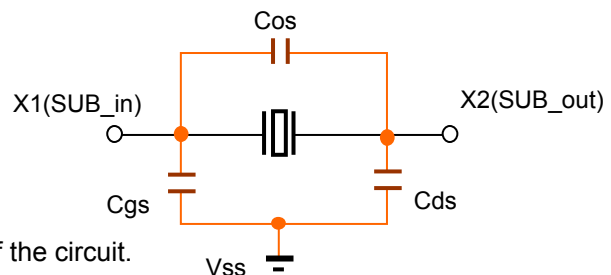Where Cs(=2 to 4pF) Stands for stray capacitance of the circuit.



Cos : X1\_X2 Stray capacitance  
Cgs : X1\_Vss Stray capacitance  
Cds : X2\_Vss Stray capacitance

Figure 4 Stray capacitance Cos,Cgs,Cds of the circuit

Resonator circuit constants will differ depending on the resonator element, stray capacitance in its interconnecting circuit, and other factors. Suitable constants should be determined in consultation with the resonator element manufacturer.